

EC6401-ELECTRONIC CIRCUITS II-QUESTION BANK**UNIT I - FEEDBACK AMPLIFIERS****PART - A (C210.1)****1. Define positive and negative feedback?**

Ans: Positive feedback: If the feedback voltage (or current) is so applied as to increase the input voltage (i.e. it is in phase with it), then it is called positive feedback.

Negative feedback: If the feedback voltage (or current) is so applied as to reduce the input voltage (i.e. it is 180° out of phase with it), then it is called negative feedback.

2. What are the advantages of negative feedback?

Ans: The advantages of negative feedback are higher fidelity and stabilized gain, increased bandwidth, less distortion and reduced noise and input & output impedances can be modified as desired.

3. List four basic types of feedback?

Ans: (1) Voltage series feedback (2) Voltage shunt feedback (3) Current series feedback and (4) Current shunt feedback.

4. Negative feedback is preferred to other methods of modifying Amplifier characteristics. Why?

Ans: Negative feedback is preferred to other methods of modifying Amplifier Characteristics because it has the following advantages of reduction in distortion, stability in gain, increased bandwidth etc.

5. State the condition in $(1+A\beta)$ which a feedback amplifier must satisfy in order to be stable.

Ans: The two important and necessary conditions are (1) The feedback must be positive, (2) Feedback factor must be unity i.e. $A\beta = 1$

6. What is meant by phase and gain margin?

Ans: Phase Margin: It is defined as 180° minus the magnitude of the $A\beta$ at the frequency at which $A\beta$ is unity. If the phase margin is negative the system is stable otherwise unstable.

Gain Margin: It is defined as the value of $(A\beta)$ in decibels at the frequency at which the phase angle of $A\beta$ is 180° . If the gain margin is negative the system is stable, otherwise the system is unstable

7. The open loop gain of an amplifier is 100. What will be the overall gain when the negative feedback of 0.5 is applied to the amplifier?

Ans: The overall gain is $A_f = \frac{A}{1 + A\beta} = \frac{100}{1 + (100 \times 0.01)} = 50$

8. List the five characteristics of an amplifier which are modified by negative feedback. (Dec-13 & May 2015)

Ans: (1) Increased stability, (2) Reduction in non-linear distortion, (3) Increased bandwidth, (4) Desensitivity of transfer Amplification & (5) Sensitivity of transfer gain

9. State the three fundamental assumptions which are made in order that the expression $A_f = A / (1 + A\beta)$ be satisfied exactly?

Ans: (1) The input signal should be transmitted to the output through the internal amplifier A and not through the feedback network. Thus if A is set to zero by reducing h_{fe} or g_m of the transistor to zero, the output must drop to zero.

(2) The feedback signal travels from the output to the input through the β network and not through the amplifier.

(3) The reverse transmission factor β of the feedback network is independent of the load and the source resistance R_L and R_s

10. State Nyquist's stability criteria for feedback amplifiers.

Ans: Nyquist's stability criterion states that in a complex S plane if $A\beta + 1$ represents a circle of unit radius with its centre at the point $-1 + j0$ and if $A\beta$ lies within the circle then $1 + A\beta < 1$, feedback is positive. Even with this positive feedback the system will not oscillate unless Nyquist criterion is satisfied.

11. What is the effect of complex loop gain and on input resistance in series voltage feedback?

Ans: In series voltage amplifier the complex loop gain decreases and the input resistance increases.

12. Mention the equation relating the gains & feedback factor in a single loop feedback amplifier.

Ans: $A_f = \frac{A}{1 + A\beta}$ (For negative feedback $A_f < A$)

$$A_f = \frac{A}{1 - A\beta} \text{ (For positive feedback } A_f > A)$$

13. Define desensitivity.

Ans: The reciprocal of sensitivity is called as de-sensitivity $D = 1 + A\beta$

Where sensitivity is defined as the fractional change in amplification with feedback divided by the fractional change without feedback and is equal to $1/(1 + A\beta)$.

14. What is the effect of voltage shunt feedback on input resistance and output resistance?

Ans: In voltage shunt feedback amplifier both the input & output resistance decrease.

15. Define trans resistance amplifier.

Ans: It is an amplifier; driven by a source represented by its Norton's equivalent i.e. the current source I_s connected with the source resistance R_s in shunt. The amplifier output circuit has been represented by its Thevenin's equivalent. This amplifier behaves as a Trans-resistance amplifier if $R_i \ll R_s$ and $R_o \ll R_L$.

16. Explain the ideal characteristics of voltage amplifier.

Ans: $R_i = \infty$, $R_o = 0$ and $V_o = A_v V_s$

17. What are the characteristics of trans-conductance amplifier?

Ans: The property of the transconductance amplifier is $R_i \gg R_s$, and $R_o \gg R_L$ and its ideal characteristics are $R_i = \infty$, $R_o = \infty$ and $I_o = G_m V_s$

18. Explain the term sensitivity.

Ans: Sensitivity is defined as the fractional change in amplification with feedback divided by the fractional change without feedback and is equal to $1/(1+A\beta)$.

19. If two stages of a multistage amplifier have gains of 20 dB and 10 dB respectively. What is the total voltage gain?

Ans: Total voltage gain = 20 + 10 = 30dB

20. Define sampling and mixing.

Ans: Sampling is the process of taking a part of output voltage or current. The process of adding or subtracting this sampled value to the input of the amplifier is called mixing.

21. Negative feedback stabilizes the gain. Justify the statement. (June-14)


Ans: The gain of the Amplifier with negative feedback is given by $A_f = A/(1+A\beta)$. When it is assumed that $A\beta \gg 1$, the above equation may be written as $A_f = A/A\beta$ i.e. $A_f = 1/\beta$. Thus, the gain of the feedback amplifier A_f has been made independent of the internal gain A . It depends only on β which in turn depends only on the passive elements such as resistors, capacitors and inductors whose values are maintained constant. And hence the gain is stabilized.

22. In a negative feedback amplifier, $A=100$, $\beta=0.04$, and $V_s=50\text{mV}$, find a) Gain with feedback, (b) Output Voltage, (c) Feedback factor (Dec13, May 16)

Ans: (a) Gain with feedback $A_f = A/(1+A\beta) = 100/(1+100 \times 0.04) = 20$

(b) Output Voltage $V_o = A_f \times V_s = 20 \times 50 \times 10^{-3} = 1000\text{mV}$.

(c) Feedback factor (β) = 0.04

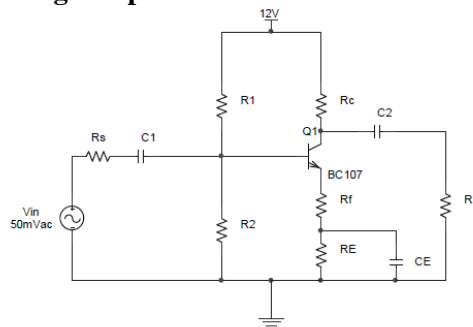23. Draw a single stage amplifier with current series feedback. (June-14)**24. Define Voltage Amplifier.**

Ans: Voltage Series feedback amplifier is called as voltage amplifier since the sampling at the output side is voltage and both the parameters in the gain are in voltage .

25. What is the other name for current series and current shunt feedback amplifier?

Ans: Current Series Amplifier is called as Transconductance amplifier and current shunt feedback amplifier is called as Current Amplifier.

26. Define 'feedback factor' of a feedback amplifier. (June-12)

Ans: Feedback factor is the fraction of the amplifier output signal which is fed back to the amplifier input. It is denoted by β .

27. State the effect on current shunt feedback on input and output resistance of the amplifier. (June-12)

Ans: The output resistance is increased and the input resistance is decreased.

28. The voltage gain without negative feedback is 40 dB. What is the new voltage gain if 3% negative feedback is introduced? (May 2015)

Ans : $\beta = 3\% = 3/100 = 0.03$; $A_v = 40$; $A_{vf} = A_v / (1 + \beta A_v) = 40 / (1 + 0.03(40)) = 18.18$

29. List the effects of negative feedback on the noise and bandwidth of an amplifier (or) What will happen for noise, if we introduce negative feedback at an amplifier. (May 16/ Nov 16, May 17)

Reduction in noise

$$N_f = N / (1 + A\beta)$$

Increase in bandwidth

$$(B.W)_f = B.W (1 + A\beta) = B.W \times D$$


30. A Negative feedback amplifier has a bandwidth of 250Khz and de-sensitivity factor of 4. What is the bandwidth of the basic amplifier without feedback. (Dec 15)

$$D = 4 ; (B.W)_f = 250 \text{ KHz}$$

$$(B.W)_f = B.W (1 + A\beta) = B.W \times D$$

$$B.W = (B.W)_f / D = 250 \times 10^3 / 4 = 62.5 \text{ KHz}$$

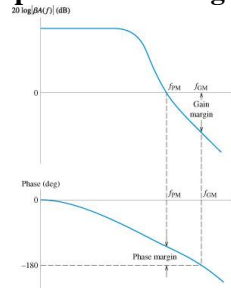31. Draw the magnitude and phase angle plot of three stage amplifier (Dec 15)



32. An amplifier has an open loop gain of 1000 and feedback ratio of 0.04. If the loop gain changes by 10% due to temperature, find the % change in gain of the amplifier with the feedback. (Nov 16)

$$\beta = 0.04; A_v = 1000; dA/A = 10\% \quad dA_{vf}/A_{vf} = (dA_v/A_v)(1/D) \quad \text{where } D = 1 + \beta A_v$$


$$= 10 (1/(1 + 0.04 \times 1000)) = 0.25\%$$

33. Mention the three networks that are connected around the basic amplifier to implement feedback concept. (May 17)


The three networks that are connected around the basic amplifier to implement the feedback concept are
 i) Mixing Network ii) Sampling Network iii) Feedback Network

PART – B (C210.1)

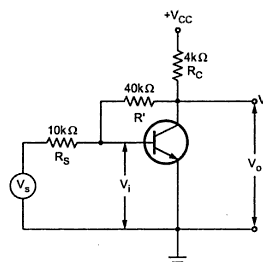1. Draw the block diagram of 4 types of feedback topologies and compare them wrt gain, input & output resistance. Give one example for each. (Dec 14)
2. Draw the circuit of an emitter follower. Identify the type of negative feedback. Calculate the gain, input & output resistance with & without feedback. (Dec 14)
3. (i) Draw the block diagram of voltage series amplifier and derive for A_{vf} , R_{if} & R_{of} . Draw a two stage amplifier with voltage series feedback. (10) (May-2015)
 (ii) Derive for bandwidth with feedback BW_f (6) (Jun 14)
4. Explain about Current shunt and Current series feedback and derive the expression for input impedance, output impedance and voltage gain. (Dec-13, May 15, Nov 16)
5. With an example circuit, explain the method of identifying the feedback topology. Also determine the feedback factor. (May 15)
6. (i) Sketch the block diagram of a feedback amplifier and derive the expressions for gain 1) With positive feedback. 2) With negative feedback. State the advantages of negative feedback. (10)
 (ii) An amplifier, with feedback, has voltage gain of 100. When the gain without feedback changes by 20% and the gain with feedback.
7. (i) What is the effect of a current series negative feedback on input resistance and output resistance of a BJT amplifier? Explain the same, with necessary circuit, equivalent circuit and equations. (8) (June-12, May 17)
8. For the amplifier circuit shown below, $h_{fe}=50$, $h_{re}=h_{oe}=0$, $h_{ie}=1.1K\Omega$. (i) Identify the topology. (ii) Obtain the basic amplifier circuit. (iii) Calculate the voltage gain, input resistance and output resistance.



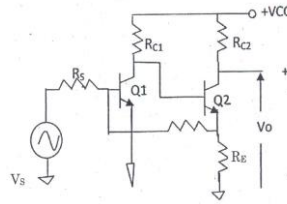9. (i) Identify the nature of the feedback in figure- 1. Let $R_{c1} = 3 \text{ k}\Omega$, $R_{c2} = 500 \Omega$, $R_E = 50\Omega$, $R_S = R_F = 1.2 \text{ k}\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1 \text{ k}\Omega$, $h_{re} = h_{oe} = 0$. Determine overall voltage gain (A_{vf}), overall current gain (A_{if}), input impedance (R_{if}) and output impedance (R_{of})



- (ii) Identify the type of feedback amplifiers shown in figure 2 (a) and 2 (b) (May – 2015)


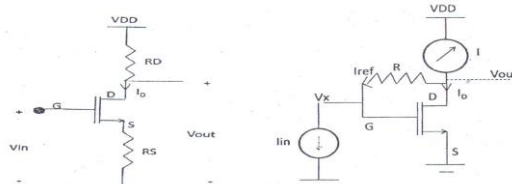



Figure 2(a)

Figure 2(b)

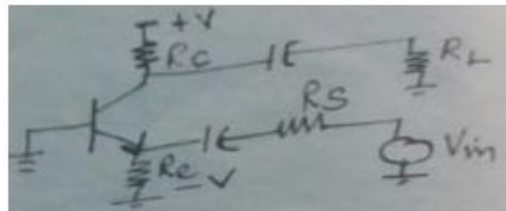10. (i) Draw the basic amplifier of the feedback amplifier shown below with equivalent circuit of basic amplifier, derive for its transfer gain and hence find its loop gain. (Dec15)



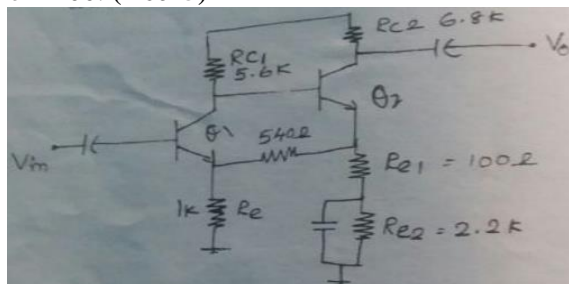- (ii) Identify the feedback topology. Find the open and closed loop gain of the circuit given. Assume $h_{ie1} = h_{ie2} = 2 \text{ k}\Omega$, $h_{fe1} = h_{fe2} = 100$. (Dec15)




11. (i) Explain in detail the stability of three pole amplifier.

- (ii) Given the loop gain function $T(f) = \beta(100)/(1+jf/10^5)^3$, determine the stability of the amplifier for $\beta = 0.2$ and $\beta = 0.02$. (Dec15)

- 12) Draw the circuit diagram of a single stage common emitter amplifier that uses emitter current feedback. Analyse the circuit and derive equations for gain, input and output impedance with feedback. (May – 2016)

- 13) With the help of a neat schematic (topology), discuss the classification of feedback amplifiers. Discuss qualitatively, the effect of topology of a feedback amplifier on input and output resistance. Also derive the expression for input and output resistance of shunt-series feedback amplifier. (May – 2016)

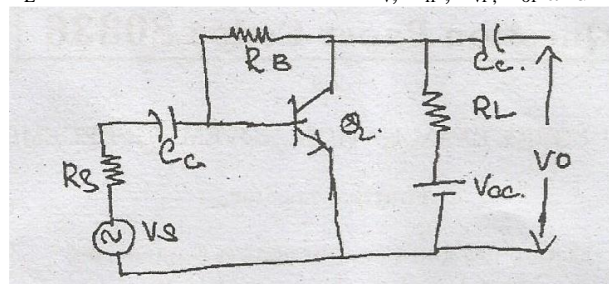- 14) Identify the feedback topology for the network shown below, which have $R_S = 600 \Omega$, $h_{ie} = 5 \text{ k}\Omega$, $h_{fe} = 80$, $R_{L1} = 2 \text{ k}\Omega$ and $R_{L2} = 2 \text{ k}\Omega$. Calculate A_v , R_{if} , A_{vf} , R_{of} and R_{of}' (Nov 16)



- 15) (i) Sketch the block diagram of a feedback amplifier and derive the expression for gain with positive feedback and with negative feedback.

- (ii) An amplifier has voltage gain with feedback as 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, determine the values of open loop gain A and feedback ratio β . (May 17)
- 16) i) Explain about voltage shunt and Current series feedback and derive the expression for input impedance, output impedance and voltage gain.
- ii) Write about the Nyquist criterion for stability of feedback amplifiers (May 17)

UNIT II - OSCILLATORS

PART – A (C210.2)

1. What are the basic mathematical conditions for sustained oscillation in an oscillator? (or) What is Barkhausen criterion? (June-12, Dec-13, June-14, May-15, May 17)

Ans: For getting sustained oscillations, the following two conditions should be satisfied. (i) The loop gain should be unity. When the loop gain is greater than unity, the amplitude of output sine wave goes on increasing exponentially. (ii) The loop phase shift should be 0° or 360° . This criterion is known as Barkhausen's criterion for oscillation

2. Explain the term "Frequency stability".

Ans: It is a measure of its ability to maintain a constant frequency over a long time Interval.

3. Classify the different sinusoidal oscillators.

Ans; A number of circuits have been used as sine wave oscillator like (i) RC oscillator, (ii) LC oscillator, (iii) Negative resistance oscillator and (iv) Crystal oscillator.

4. What is a resonant circuit oscillator?

Ans: The Oscillators using resonant LC tank circuits are most often used for sources of radio frequency (RF) energy are called as resonant circuit oscillator.

5. What are the factors needed to choose type of oscillators?

Ans: The factors needed to choose type of oscillators are (i) The nature of generated wave form, (ii) The frequency of generated signals, (iii) The type of associated circuit of components and (iv) The fundamental mechanism involved.

6. Give the condition of oscillation for Hartley oscillator.

Ans: The condition of oscillation for Hartley oscillator is

$$h_{fe} = \frac{X_1}{X_2} = \frac{L_1 + M}{L_2 + M}$$

7. What is the difference between amplifier and oscillator? (Dec-13)

Ans: In an amplifier circuit, the frequency, waveform, and magnitude of a.c power generated is controlled by a.c signal voltage applied at the input of the amplifier. On the other hand in an oscillator, the frequency, waveform, and magnitude of a.c power generated is controlled by the circuit itself i.e. no external controlling voltage is required. Thus an oscillator may be considered as an amplifier which provides its own input signal.

8. In a feedback amplifier, explain how oscillation takes place by deriving A_f (Gain with feedback).

Ans: The function of the feedback circuit is to transfer a part of the output energy to the input in proper phase. When the feedback is positive, the overall gain of the amplifier is written as

$$A_f = \frac{A}{1 - A\beta} \text{ Where } A\beta \text{ is feedback factor or loop gain.}$$

If $A\beta = 1$, $A_f = \infty$. Thus the gain becomes infinity i.e. there is output without any input. Thus the amplifier works as an oscillator and the oscillation will take place.

9. Why RC phase shift oscillators are needed?

Ans: For the generation of low frequency signals, the LC circuits become impracticable and the RC phase shift oscillators are more suitable. With the advantage of IC technology RC network is the only feasible solution. It is very difficult to make an inductance that too of very high value in an IC. Therefore RC oscillators are increasingly popular.

10. Which oscillator uses both positive and negative feedback? Why?

Ans: Wien bridge oscillator uses both positive and negative feedback. The positive feedback ensures sustained oscillation, the negative feedback ensures constant output i.e. any increase or decrease in the oscillator output is taken care of by this negative feedback.

11. What are the advantages of crystal oscillator?

Ans: (i) Simple circuit since no tuned circuit is needed other than the crystal it-self is used.

(ii) Different frequencies of oscillations can be obtained by simply replacing one crystal another. Hence it makes it easy for a radio transistor to work at different frequencies.

(iii) Since the frequency of oscillation is set by the crystal, changes in the supply V_g and transistor parameters does not affect the frequency of oscillation.

12. How oscillations occur in a crystal oscillator?

Ans: When an alternating voltage is applied, the crystal starts vibrating with a frequency of applied voltage. If the frequency of applied voltage is made equal to the natural frequency of crystal, resonance takes place and crystal vibrates and the oscillations occur with maximum amplitude.

13. Name two low frequency oscillators.


Ans: (i) RC phase shift oscillator, (ii) Wein bridge oscillator.

14. Name two high frequency oscillators.

Ans: (i) Hartley oscillator, (ii) Colpitts oscillator.

15. Draw an electrical equivalent circuit for a quartz crystal. (Dec-13, June-14)

Ans:

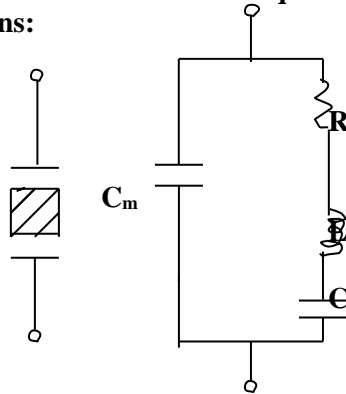

Where **R = Mechanical friction**

C = Mechanical Compliance

L = Mass of the vibrating crystal

16. Give the frequency ranges over, which the tunnel diode oscillator is employed.

Ans: 20 GHz to 100 GHz (in the microwave frequency range)

17. Why L-C oscillators are not preferred to generate low frequency signals even though they have higher frequency stability compared to R-C phase shift oscillator?

Ans: For the generation of low frequency signals, the LC circuits become impracticable and the RC phase shift oscillators are more suitable. With the advantage of IC technology RC network is the only feasible solution. It is very difficult to make an inductance that too of very high value in an IC. Therefore RC oscillators are increasingly popular.

18. Write the expression for frequency of oscillation in RC-phase shift oscillator.

Ans:

$$f_o = \frac{1}{2\pi RC\sqrt{6+4K}} \quad \text{where } A_f = \frac{R_c}{R}$$

19. Why crystal oscillators are superior to other oscillators?

Ans: Crystal oscillators are superior to other oscillators because of their great mechanical strength, simplicity of manufacture and it obeys the piezoelectric effect accurately.

20. What is meant by un-sustained oscillation? When it will occur?

Ans: The electrical oscillations whose amplitude goes on decreasing with time are called un-sustained oscillation. The electrical system in which these oscillations are generated has losses and some energy is lost during each oscillation. Further, no means are provided to compensate for the losses and consequently the amplitude of the generated wave decreases gradually.

21. What is the expression for frequency of oscillation in Weinbridge oscillator?

Ans: $f_r = \frac{1}{2\pi RC}$

22. In a Hartley oscillator, if L1=0.2mH, L2=0.3mH and C=0.003μF. Calculate the frequency of oscillation. (June-12, May 17)

Ans: The total inductance $L=L_1+L_2=0.5\text{mH}$. Frequency of oscillation can be calculated using the formula

$$f_r = \frac{1}{2\pi\sqrt{LC}}. \text{ Therefore } f_r = \frac{1}{2\pi\sqrt{0.5 \times 10^{-3} \times 0.003 \times 10^{-6}}} =$$

23. What is lead-lag network?

Ans: Compensating network which combines the characteristics of the lag and lead networks, and in which the phase of a sinusoidal response lags a sinusoidal input at low frequencies and leads it at high frequencies. Also known as lag-lead network.

24. A Weinbridge oscillator is used for operations at 9 KHz. If the value of the resistance R is 100 KΩ, what is the value of C required? (June-12)

Ans: The frequency of operation for Weinbridge oscillator is given by $f_r = \frac{1}{2\pi RC}$. Therefore the value of C can be obtained as follows.

$$C = (f_r \times 2\pi \times R)^{-1} = (2\pi \times 9 \times 10^3 \times 100 \times 10^3)^{-1} = 0.174 \text{ nF.}$$

25. A tuned collector oscillator in a radio receiver has a fixed inductance of 60μH and has to be tunable over the frequency band of 400KHz to 1200KHz. Find the range of variable capacitor to be used. (June-12)


Ans: Frequency of oscillation is given by $f = \frac{1}{2\pi\sqrt{LC}}$. Therefore, $C = \left(\frac{1}{2\pi\sqrt{L}f}\right)^2$. For f=400KHz,

C=7.16 mF and for f=1200KHz, C= 4.13 mF.

26. Write the feedback factor expression for BJT based Wein bridge oscillator.

$Z_1 / (Z_1 + Z_2)$ where $Z_1 = R_1 / 1 + j\omega R_1 C_1$; $Z_2 = R_2 + 1 / j\omega C_2$

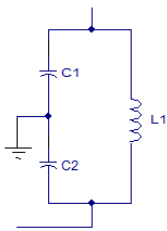27. Sketch the feedback circuit of a Colpitts Oscillator. Calculate the value of the equivalent series capacitance required if it uses an inductance of 100mH and is to oscillate at 40Khz. . (May 16)



$f = \frac{1}{2\pi\sqrt{LC}}$ Where L is the inductance of the inductor in the tank circuit and C is

the effective capacitance of the capacitors in the tank circuit. If C1 and C2 are the individual capacitance, then the effective capacitance of the serial combination $C = (C1 * C2) / (C1 + C2)$. Here substitute $F = 40 \times 10^3$ Hz and $L = 100 \times 10^{-3}$ H. Calculate C. $C = 0.01 \text{ mF}$

28. Mention the advantages and disadvantages of RC phase shift oscillators. (May 16 / Nov 16)

Ans: Advantage : For the generation of low frequency signals, the LC circuits become impracticable and the RC phase shift oscillators are more suitable. With the advantage of IC technology RC network is the only feasible solution. It is very difficult to make an inductance that too of very high value in an IC.

Disadvantage: The output is small and It is due to smaller feedback. The frequency stability is not as good as that of the Wien bridge oscillator. It is difficult for the circuit to start oscillations as the feedback is usually small

29. The quartz crystal has $C_m = 1 \text{ pF}$, $L_s = 3 \text{ H}$, $C_s = 0.05 \text{ pF}$ and $R_s = 1 \text{ k}$. Calculate the series and parallel resonant frequencies. (Dec 15)

$$C_{eq} = C_m C_s / C_m + C_s = 0.0476 \text{ F}$$

$$f_s = 1 / 2\pi \sqrt{L_s C_{eq}} \\ = 0.06 \text{ Hz}$$

$$f_p = 1 / 2\pi \sqrt{L_s C_m} \\ = 0.02754 \text{ } \mu\text{f}$$

30. How Barkhausen conditions are satisfied in Twin-T Oscillator? (Dec 15)

The phase shift introduced in the feedback loop of two T – Network is 0, and the gain of the amplifier is 3.

31. What are the factors which affect the frequency stability of an oscillator? (Nov 16)

- Operating point
- Interelment capacitances
- Stray capacitances
- Temperature
- Circuit components
- Gain (β)
- Supply voltages

PART-B (C210.2)

- With a neat diagram explain about RC phase shift oscillator using BJT and derive the expression for frequency of oscillation and condition of oscillation. Also discuss about frequency stability of an oscillator (June-12, Dec-13, June-14, May-2015)
- With a neat diagram explain about Wien Bridge oscillator and derive the expression for frequency of oscillation and condition of oscillation. (May 15, Dec 15)
- With a neat diagram explain about Colpitt oscillator & derive the expression for frequency of oscillation and condition of oscillation. (June-14, May 15, Dec 15, May 17)
 - Design a clap oscillation to generate 12Khz Sine wave using BJT amplifier with a gain of 110. Given $g_m = 30 \text{ mA/V}$, $h_{fe} = 150$. Draw the designed circuit $V_{ec} = 20 \text{ V}$. (Dec 15)
- Explain the drawback of Colpitt oscillator and how it is overcome in Clapp oscillator (June-14).
- With a neat diagram explain about Hartley oscillator & derive the expression for frequency of oscillation and condition of oscillation. (Dec-13)
 - In colpitt's oscillator $C_1 = 1 \text{ } \mu\text{F}$ and $C_2 = 0.2 \text{ } \mu\text{F}$. If the frequency of oscillation is 10 kHz, find the value of inductor. Also find the required gain for sustained oscillation. (May-2015)

6. With a neat diagram explain about Clapp oscillator & derive the expression for frequency of oscillation and condition of oscillation.
7. Define piezoelectric effect. Draw the equivalent circuit of quartz crystal oscillator.
8. Explain about pierce crystal oscillator.
9. (i) Draw Hartley oscillator using FET, explain & derive the condition for oscillation
(ii) Briefly discuss about the frequency of oscillation of Franklin oscillator (4)
(iii) Write an advantage of Wein bridge oscillator over RC – phase shift oscillator. (2) **(May 15)**
10. With neat circuit diagram, explain the working principle of the following oscillators. (i) Tuned collector oscillator, (ii) Franklin oscillator, (iii) Armstrong oscillator. **(June-12, Nov 16)**
11. Derive the frequency of oscillation of a Wein bridge oscillator. With the circuit diagram of its discrete version (using BJTs), explain how Barkhausen condition are satisfied in Wein bridge oscillator.
12. (i) Explain the principle of operation of Armstrong oscillator with neat circuit diagram.
(ii) Discuss the operation and the principles involved in Twin – T Oscillators. **(May 16)**
13. (i) Discuss briefly the principle of oscillation in crystals and draw the equivalent circuit, impedance frequency graph of crystals give expression for its series and parallel resonant frequency.
(ii) Discuss about the frequency stability of crystal oscillator. **(May 16)**
14. Derive the general form for frequency of oscillation for LC oscillator with suitable diagram **(Nov 16)**
15. i) Sketch the circuit of a phase shift oscillator and explain its design approach
ii) A Colpitt oscillator is designed with $C_1 = 100\text{pF}$, $C_2 = 500\text{pF}$ and $L = 40\text{ mH}$. Find the frequency of oscillation. **(May 17)**

UNIT III – TUNED AMPLIFIERS

PART – A(C210.3)

1. What are Band pass amplifiers?

Ans: Band pass amplifiers are nothing but tuned amplifiers which are used to select a desired RF signal and to amplify the selected RF signal to a suitable level.

2. What is the need of output matching Transformer?

Ans: The single tuned amplifiers will give the impractical values of the circuit components and low gain because of the low effective resistance in the base or input circuit of the transistor. It can be avoided by using a tapped inductor as an auto transformer. This serves effectively to transform the low effective resistance into a more reasonable value

3. Define Q.

Ans: Q is Quality factor. It is defined as the measure of the quality of the tuned circuit and is the ratio of inductive reactance to the resistance of the coil at resonance.

4. Comment on Gain-Bandwidth product of a tuned amplifier.

Ans: This is the figure of merit defined in terms of mid band gain and the bandwidth of the tuned amplifier.

5. Explain the concept of Impedance matching.

Ans: The single tuned amplifiers will give the impractical values of the circuit components and low gain because of the low effective resistance in the base or input circuit of the transistor. It can be avoided by using a tapped inductor as an auto transformer. This serves effectively to transform the low effective resistance into a more reasonable value.

6. Differentiate between single and stagger tuned amplifier.

Ans: single tuned amplifier uses one parallel tuned circuit as the load impedance in each stage and all these tuned circuits in different stages are tuned to the same frequency but the staggered tuned amplifier uses a number of single tuned stages in cascade, the successive tuned circuits being tuned to slightly different frequencies.

7. What is effective Quality factor?

Ans: The effective quality factor or the circuit magnification factor of the output circuit at resonant frequency ω_r is given by

$$Q_{eff} = \frac{\text{Susceptance of inductance L or Capacitance C}}{\text{Conductance of shunt resistance}} = \frac{R_t}{\omega_f L} = \omega_r C_{eq} R_t$$

8. Define loaded and unloaded Q.

Ans: Unloaded Q: It is the ratio of energy stored to the energy dissipated in a reactor.

Loaded Q: It is defined as how tightly the resonator is coupled with the terminations.

9. What is a stagger-tuned amplifier?

Ans: If two or more tuned circuits are cascaded and are tuned to slightly different frequencies, it is possible to obtain an increased bandwidth with flat pass band with steep sides. The tuned amplifier used to do this is called as stagger tuned amplifier.

10. What is a synchronous tuned amplifier?

Ans: A number of amplifiers can be cascaded in order to achieve high gain. All stages are assumed to be identical and to be tuned to the same frequency. This is termed as synchronously tuned amplifier which has increased gain and band width which is narrower than the band width of each of the stages.

11. What is the effect of ‘Q’ on stability?

Ans: Higher the value of Q, provides better stability, but smaller bandwidth and larger gain. Hence it provides less stability.

12. Define coil losses.

Copper loss, Eddy current loss and hysteresis loss are called coil losses.

13. What is the instability of tuned amplifiers?

Due to the internal capacitance between the input and output there will be feedback in the circuit. If the feedback is positive then the circuit starts oscillating instead of amplifying.

14. What is the advantage of stagger tuning?

Ans: It increases the bandwidth with a flat pass-band with steep sides.

15. What are the techniques of stabilizing a band pass amplifier?

Ans: (i) Neutralization, (ii) Unilaterization, (iii) Mismatching technique.

16. What is Neutralization? (Dec-13, June-14, Dec15)

Ans: At high frequencies the various capacitances of the transistor circuits play an important role. If some feedback signal manages to reach the input terminal as a positive feedback, the stability of the circuit is affected. To avoid this, a capacitance is connected in the feedback circuit to neutralize the effect of other capacitances. This is called Neutralization.

17. Write the disadvantages of tuned amplifier. (June-12)

Ans: (1) Since they use inductors & capacitors as tuning elements, the circuit is bulky and costly, (2) If the band of frequency is increased, design becomes complex. (3) They are not suitable to amplify audio frequency.

18. Write the advantages of tuned amplifier. (June-12)


- Ans: 1. They amplify desired frequencies.
- 2. Signal to noise ratio at output is good.
- 3. They are well suited for radio Transmitters and receivers.
- 4. The band of frequencies over which amplification is required can be varied.

19. What are tuned amplifiers? What are the various types of Tuned simplifiers? (Dec-13)

Ans: Amplifiers which amplify a specific frequency or narrow band of frequencies are called tuned amplifiers. The types are (i) Single tuned amplifiers, (ii) Double tuned amplifiers and (iii) Stagger tuned amplifiers.

20. Draw the frequency response of single tuned amplifier.

Ans:

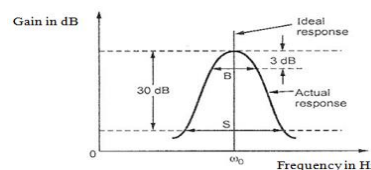

21. What are the applications of tuned amplifiers?

Ans: (i) Selection of a desired radio frequency signal. (ii) Amplification of the selected signal to a suitable voltage level.

22. Define double-tuned voltage amplifier.


Ans: A tuned amplifier, which has two resonance circuits (i.e. LC circuit) and shows wider bandwidth.

23. Determine the bandwidth of two stage synchronous tuned amplifier. Assume the bandwidth of individual stage is 310 kHz. (May -2015)


$$BW_2 = BW \sqrt{2^{1/N} - 1} = 310 \sqrt{2^{1/2} - 1} = 200$$

24. Draw a Double tuned amplifier and its frequency response for different kinds of coupling. (June-14)

Ans:

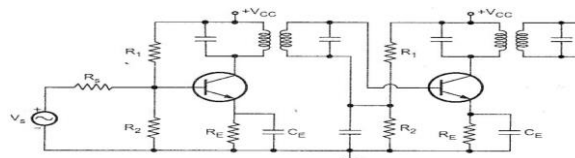


Frequency Response:

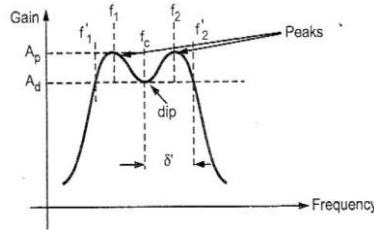


25. A tuned circuit has resonant frequency of 1600KHz and bandwidth of 10KHz. What is the value of Q factor? (June-12, May 17)

$$\text{Since } \text{Bandwidth} = \frac{f_o}{Q}, Q = \frac{f_o}{BW} = \frac{1600\text{KHz}}{10\text{KHz}} = 160$$

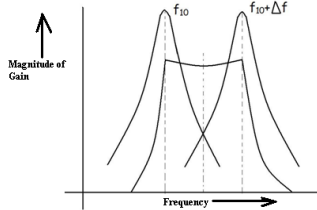26. Draw the frequency response of stagger tuned amplifiers.



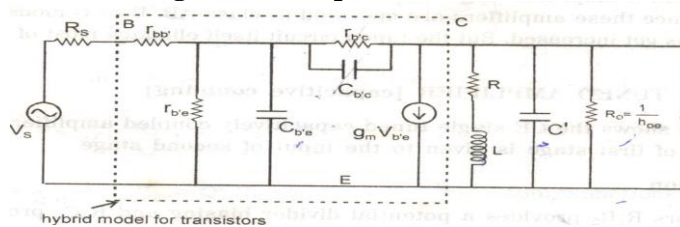
27. Draw the small signal model of a single tuned amplifier.



28. What is the effect of Q on the resonance circuit? (May 16)

Q factor is a dimensionless parameter that describes how under - damped an oscillator or resonator is, and characterizes a resonator's bandwidth relative to its center frequency. Higher Q indicates a lower rate of energy loss relative to the stored energy of the resonator; the oscillations die out more slowly. Resonators with high quality factors have low damping so that they ring or vibrate longer.

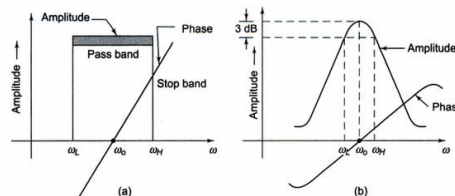29. Draw the ideal response and actual response of tuned amplifier (May 16)



(a) Ideal response

(b) Actual response

30. A 3μH coil used in tuned amplifier tunes to 1050 KHz has R_s of 50Ω. If the load resistance of the amplifier is R_L=5k. Calculate the loaded and unloaded Q of the tank circuit. (Dec 15)

$$\text{Unloaded } Q = \omega_0 L / R_s$$

$$R_s = 50 \Omega; L = 3\mu\text{H}$$

$$\omega_0 = 2\pi \times 1050 \times 10^3 = 6597\text{KHz}$$

$$\text{Loaded } Q = \omega_0 L / R$$

$$R = R_s \parallel R_L; R_L = 5\text{k}$$

31. List out some advantages of double tuned amplifier. (Nov 16)

1. It provides larger 3 dB bandwidth than the single tuned amplifier and hence provides the larger gain-bandwidth product. 2. It provides gain versus frequency curve having steeper sides and flatter top

32. Define Q factor of the capacitor. (Nov 16)

The Q-factor or the quality factor of a capacitor at the operating frequency ω is defined as the ratio of the reactance of the capacitor to its series resistance. Quality factor $Q = 1 / \omega CR$

33. An inductor of 250 micro Henry has Q = 300 at 1 MHz. Determine R_s and R_p of the inductor (May 17)

$$R_s = \omega_0 L / Q = (2\pi \times 1 \times 10^6 \times 250 \times 10^{-6}) / 300, R_p = \omega_0 L * Q = (2\pi \times 1 \times 10^6 \times 250 \times 10^{-6}) \times 300$$

PART-B(C210.3)

1. With a neat diagram explain the operation of single tuned amplifier and derive the expression for gain, gain bandwidth product and frequency of oscillation. **(Dec-13, June-14, May-2015)**
2. With a neat diagram explain the operation of synchronously tuned amplifier and derive the expression for gain. **(or)** Discuss the effect of cascading single tuned amplifier on bandwidth (**Nov 16**)
3. What is the instability of tuned amplifiers? Explain about the different stabilization techniques. **(Dec-13)**
4. With a neat diagram explain the operation of Class – C tuned amplifier and derive the expression for efficiency of the same. **(June-14, May-2015, Dec 15. Nov 16, May 17)**
5. With a neat diagram explain the operation of inductively coupled single tuned amplifier and derive the expression for gain & gain bandwidth product.
6. With a neat diagram explain the operation of capacitively coupled single tuned amplifier and derive the expression for gain and gain bandwidth product. **(June-12)**
7. Explain the working of stagger tuned amplifiers with derivations. **(Dec-13, June-14)**
8. Discuss the effect of cascading tuned amplifiers. **(Dec-13)**
9. (i) List out the neutralization techniques that are used in the stability of tuned amplifier. With the help of neat circuit diagram explain anyone
(ii) Explain the frequency response of stagger tuned amplifier (**May-2015**).
10. Describe the operation of a capacitance coupled single tuned amplifier and analyse the circuit with the high frequency transistor model to obtain the gain and bandwidth of the amplifier. Sketch its frequency response. (**May-2016**).
11. Discuss briefly the need for neutralization in tuned amplifiers. Explain Hazeltine and neutrodyne neutralization methods with relevant circuit diagrams. (**May-2016**).
12. (i) Why Neutralization is needed in tuned amplifier. Explain Hazeltine neutralization with circuit diagram. **(Nov 16, May 17)**
(ii) With circuit diagram and small signal equivalent circuit, derive expression for selectivity Characteristics $A_{(v)}/A_{vmax}$ of single tuned amplifier. Also derive for its 3dB cut-off frequencies **(Dec15)**
13. i) Draw the circuit diagram of a double-tuned voltage amplifier and explain how its frequency response is better than that of a single-tuned voltage amplifier with the expression for 3dB bandwidth (**May 17**)
14. Design a tuned amplifier using FET to have $f_0 = 1$ MHz, 3 dB bandwidth is to be 10 KHz and maximum gain is to be -10. FET has $g_m = 5$ mA/V and $r_d = 10$ K Ω **(May 17)**

UNIT IV - WAVE SHAPING AND MULTIVIBRATOR CIRCUITS

PART – A(C210.4)

1. What is meant by a switching circuit?

Ans: A circuit which can turn ON or OFF current in the electronic circuit is known as switching circuit. It can be used to produce non-sinusoidal waves like square, rectangular and saw tooth waves. (e.g.) Multivibrators.

2. What is a Multivibrator?

Multivibrator is basically a two stage amplifier with output of one supplied back to the input of the other. It is a switching circuit and may be defined as an electronic circuit that generates non sinusoidal waves.

3. What are the different types of Multivibrators?(Nov 16)

Ans: There are three types of multivibrator circuits in use namely (a) Astable Multivibrator (b) Monostable Multivibrator (c) Bistable Multivibrator

4. What is Astable Multivibrator?

Ans: Astable Multivibrator has no stable state. There are two quasi stable states. The circuit changes automatically from one quasi stable state to another quasi stable state without any triggering. The rate depends upon the RC time constants in the circuit. Thus it is just an oscillator since it does not require any external pulse for its operation.

5. Why do we call Astable Multivibrator as free running Multivibrator?(May 17)

Ans: As this Multivibrator does not require any external pulse for the transition, is called free running Multivibrator.

6. Explain the stable state of a Multivibrator.

Ans: The condition in which the multivibrator may remain indefinitely until the circuit is triggered by some external signal is termed as the stable state.

7. What is the frequency of oscillation of Astable multivibrator?

Ans: Time period $T = 1.39 RC$

Frequency of oscillation $f = 1/T = 1/1.39 RC = 0.7/RC$

8. What is storage time delay?

Ans: On the application of a reverse bias to the base of the transistor in saturation, a small interval of time is required to draw the stored charge out of the base of a transistor before the collector current starts changing. This delay is called Storage time delay.

9. What are the applications of Astable multivibrator?

- (1) It can be used as square wave generator and voltage-frequency Converter
- (2) Used as clock for binary logic signals.
- (3) Used in the construction of digital voltmeters and SMPS.
- (4) Used to generate signals over a wide range of audio and radio frequencies.

10. Define Monostable Multivibrator.

Ans: When a trigger pulse is applied to the input circuit the circuit stable state is changed abruptly to quasi stable state for a predetermined time after which the circuit returned to its original stable state automatically.

11. What is the frequency of oscillation of Monostable Multivibrator?

Ans: Time period $T = 0.69RC$

Frequency of oscillation $f = 1/T = 1/(0.69 RC)$

12. Which Multivibrator would function as time delay unit? Why?

Ans: Monostable Multivibrator is used as a time delay unit since it produces a transition at a fixed time after the trigger signal.

13. Why the Bistable Multivibrator is also called Flip Flop Multivibrator?

Ans: The Bistable Multivibrator is also known as Flip Flop Multivibrator. The reason is that one triggering pulse causes the Multivibrator to 'Flip' for one stable state to another stable state while the second pulse causes it to 'Flop' back to the original stable state.

14. What is settling time in a Multivibrator?

Ans: The Voltage across the commutating capacitors does not change during transition time. This takes place after the transition time. The time needed for this recharging or discharging of these capacitors after the transfer of conduction has been completed is called settling time.

15. What is the function of commutating (Transpose) Capacitors in Bistable Multivibrator? (May-2015, May 16)

Ans: A Bistable Multivibrator remains in one of its stable states until a triggering pulse is applied. After the application of this triggering pulse, the time taken for the transistor to transfer from ON state to OFF state is called transition time. This transition time should be as small as possible and to speed up the transition, capacitors are used in shunt with the coupling resistors. These capacitors are called speed up capacitors or commutating capacitors or transpose capacitors.

16. What are the applications of Bistable Multivibrator?

- Ans: (1) It can be used to perform digital operations like counting and storing of digital information.
 (2) Used as memory element in shift registers, counters etc.
 (3) Used in processing of pulse type waveform.
 (4) Used as frequency divider.

17. Under what condition would a Schmitt operate as an amplifier?

Ans: The collector resistance R_{c1} is kept enough smaller than R_{c2} so that regeneration cannot take place. This is the condition at which the Schmitt trigger can be used as an amplifier.

18. What is meant by hysteresis in a Schmitt Trigger?

Ans: In a Schmitt Trigger, the response curve between the input and output voltages varies with loop gain when the loop gain is greater than unity, the output voltage increases with decrease in input voltage between two points. When UTP is reached, the circuit changes its state but V_i decreases. This produces an S type curve and this is known as hysteresis.

19. Explain lower and upper triggering voltages in Schmitt Trigger.

Ans: UTP: (Upper Trigger Point) is the point at which the transistor enters into conduction. i.e. OFF to ON state.

LTP: (Lower Trigger Point) is the point at which the transistor enters from ON to OFF state.

20. State the applications of Schmitt Trigger. (June-12 / Nov 16)

Ans: (1) Amplitude Comparator, (2) As a Flip Flop and (3) As a squaring circuit.

21. What is an integrator?

Ans: In some RC circuits, Capacitor C stores some of the charge on each cycle .i.e. it integrates or adds the charges on each pulse until it becomes charged to some definite value. RC circuits used to integrate pulses are called RC integrator circuits or low pass circuits.

22. What is differentiator?

Ans: In some RC circuits, the waveform of the voltage across the capacitor is substantially the same as that of the applied voltage, where as the voltage across the resistors has a new waveform which is dependent

upon how fast the applied voltage changes. Because of their ability to differentiate between rates of change of the applied voltage, these circuits are called differentiator circuits. Also they are called High pass filters.

23. Define the threshold points in a Schmitt Trigger circuit. (Dec-13)

Ans: The Schmitt Trigger is a type of comparator with two different threshold voltage levels. Whenever the input voltage goes over the High Threshold Level, the output of the comparator is switched HIGH (if is a standard ST) or LOW (if is an inverting ST). The output will remain in this state, as long as the input voltage is above the second threshold level, the Low Threshold Level. When the input voltage goes below this level, the output of the Schmitt Trigger will switch.

24. Determine the value of capacitors to be used in an astable multivibrator to provide a train of pulse of 4µs wide at a reception rate of 80 KHz if R1=R2=10 KΩ. (Dec-13)

Ans: The period of oscillation is given by $T = 1/f = (1/80 \times 10^3) = 12.5 \mu s$

$T1 = 4 \mu s$ (Given), $T2 = T - T1 = 12.5 - 4 = 8.5 \mu s$

$T1 = 0.693 R1 C1$, therefore $C1 = T1 / (0.693 R1) = 577 \text{ pF}$

$T2 = 0.693 R2 C2$, therefore $C2 = T2 / (0.693 R2) = 1.226 \text{ nF}$

25. Briefly explain any one type of triggering for Bistable multivibrator (June-14)

Ans: Let us assume that initially transistor Q1 is ON and Q2 is OFF in the Bistable multivibrator. It is a stable state of the circuit and it will remain in this state until a trigger pulse is applied from outside. A positive triggering pulse applied to the reset input (base of Q2) increases its forward bias, thereby turning transistor Q2 ON and an increase in collector current and a decrease in collector voltage. The fall in collector voltage is coupled to the base of Q1, where it reverse biases the base-emitter circuit and Q1 is thus turned OFF. The circuit is then in its second stable state and remains so till a positive trigger pulse is applied to set input (base of Q1).

26. What is meant by clamper circuit? (June-12)


Ans: A clamping circuit is used to place either the positive or negative peak of a signal at a desired level. The dc component is simply added or subtracted to/from the input signal.

27. Differentiate between Clipper and Clamper circuits (May-2015)


Ans

CLIPPERS	CLAMPERS
Clips a portion of a waveform depending upon the applied reference voltage	Clamps or adds the required dc level to the applied input AC signal
Also called as slicer or limiter	Also called as DC inserter or restorer

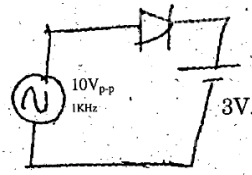28. Draw the input and output waveform of the circuit shown below (June-14)



Ans:

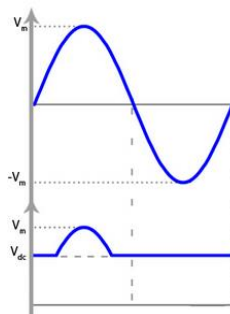

29. An RC low pass circuit has R=1.5kΩ and C=0.2µf. What is the rise time of the output when excited by a step input. (May 16)


3 db cut – off frequency : $f_h = 1/2\pi RC = 530 .51 \text{ Hz}$

Rise time : $t_r = 0.35/ f_h = 6.59 \times 10^{-4} \text{ sec.}$

30. Define rise time of a switching transistor. (Dec 15)

Ans: It is the time taken for the output to rise from 10% to 90 % of its steady state value. Rise time depends upon the input capacitance. During rise time t_r , Collector-emitter voltage falls from V_{CC} to V_{CES}

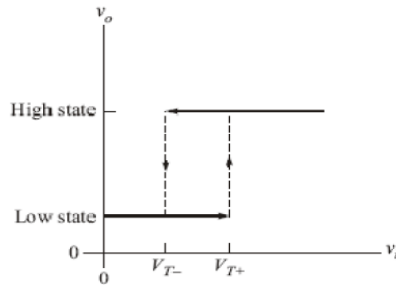31. Draw the hysteresis characteristics of the Schmitt trigger circuit. (Dec15)




32. How can a Schmitt trigger act as a zero crossing detector? (May 17)

A Schmitt trigger circuit is also called a regenerative comparator circuit. The circuit is designed with a positive feedback and hence will have a regenerative action which will make the output switch levels. Also, the use of positive voltage feedback instead of a negative feedback, aids the feedback voltage to the input voltage, instead of opposing it. The use of a regenerative circuit is to remove the difficulties in a zero-crossing detector circuit due to low frequency signals and input noise voltages.

PART-B(C210.4)

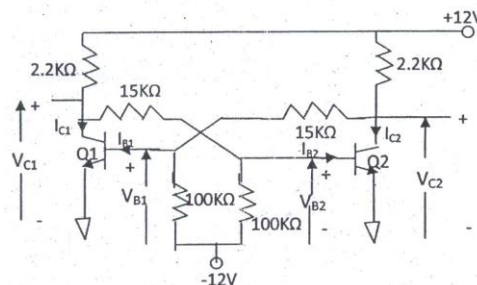1. i) Draw the circuit of emitter coupled astable multivibrator for one of the quasi stable states and show the direction of currents. Mention the terminal voltages in the circuit.
 ii) With a neat diagram explain the working of monostable multivibrator. Derive it's on time. Draw the base and collector signals. (Nov 16)
2. Design a collector coupled astable multivibrator for the following specifications: output voltage = 10V, $I_c = 1\text{mA}$, $h_{fe} = 100$, $I_{cbo} = 0$, output to be a positive pulse, the duration of which is 20µsec, the time between pulses to be 10µsec.
3. Sketch the response of RC high pass filter for the following inputs and explain (i) Ramp and (2) Pulse. (Dec-13)
4. Explain the switching characteristics of transistor with neat sketch. (Dec-13, May 17)
5. Explain with a neat diagram the operation of types of clampers and draw the output waveform. (June-14)
6. With a neat diagram explain the operation of collector coupled Astable multivibrator and derive the expression for frequency. (June-14, Dec-15)
7. With a neat diagram explain the operation of collector coupled Bistable multivibrator (May 17)
8. With a neat diagram explain the triggering methods of Monostable multivibrator.
9. Design a discrete monostable multivibrator with $V_{cc} = 20\text{V}$ and $T = 5\text{ sec}$. Draw the designed circuit. (June-14)
10. (i) Design a Schmitt trigger using BJT with $UTP = 5\text{ v}$ and $LTP = 2\text{v}$. Assume $V_{cc} = 15\text{ v}$, $I_{c2} = 5\text{ mA}$ and $h_{fe} = 100$ (May-2015)
 (ii) Consider a fixed bias NPN bistable multivibrator shown in figure 3. Determine its stable currents ($I_{B1}, I_{C1}, I_{B2}, I_{C2}$) and stable voltages ($V_{B1}, V_{C1}, V_{B2}, V_{C2}$) when Q_1 is on ON and Q_2 is on OFF



11. Explain the operation of a Schmitt Trigger with a neat circuit diagram showing relevant input and output waveforms. (May-2016)
12. Explain the following: (i) Positive clamper (ii) Negative clamper and (iii) RC circuit differentiator (May-2016)
13. (i) Explain a clamper and clipper circuit with input and output waveforms
 (ii) With switching characteristics of BJT, explain the cause of storage, rise, delay, off times and how they can be reduced to improve the switching time of BJT (Dec-15)
14. Design a saturated collector coupled multivibrator for the following specification. Output voltage 12V peak. Output to be positive pulse, the duration is 10 micro seconds. The time between pulses to be 20 micro seconds, for the BJT $h_{fe} = 100$, $I_{CBO} = 0$, $I_{C(ON)} = 1\text{mA}$, assume $V_{CE(sat)} = 0.2\text{V}$ (Nov 16)
15. Design a Astable multivibrator circuit to generate a pulse waveform at 40% duty cycle at 20 KHZ using $V_{cc} = 10\text{V}$, $h_{fe} = 220$, $I_{C(sat)} = 2\text{ mA}$ (May 17)

UNIT V - BLOCKING OSCILLATORS AND TIMEBASE GENERATORS**PART – A (C210.5)****1. What are Blocking Oscillators?**

Ans: The Blocking Oscillator is a special type of relaxation oscillator which produces a single pulse as output or a train of pulses. This is achieved by a regenerative feedback amplifier using a transistor where the feedback is through a pulse transformer.

2. What are the different modes of blocking oscillators?

Ans: There are two major modes of operation – the monostable or triggered mode which produces a single pulse output and the astable mode which produces a pulse train.

3. What are the uses of a pulse transformer? (June-12)

Ans: A pulse transformer is used for satisfying any one of the following requirements (1) Isolation between signals, (2) A floating source, (3) A coupling circuit between stages and (4) Stepping up or downing the signals.

4. Classify the different types of Blocking oscillators.

Ans: 1. Monostable Blocking oscillators (Base time and Emitter time)

2. Astable Blocking Oscillators (Diode Controlled and RC Controlled)

5. How do we avoid distortion in the output of a pulse transformer?

Ans: The distortion can be avoided by making magnetising inductance (L) very high and Leakage inductance (σ) and Capacitance (C) very low during design.

6. What are the applications of Blocking oscillator? (May 16)

Ans: (i) used as frequency divider or counter.

(ii) used as low impedance switch

(iii) used as master oscillator to supply triggering signals for synchronizing the system.


7. What is the equation for the coefficient of coupling in a pulse transformer?

Ans: The coefficient of coupling for this type of transformer is unity. The coefficient of coupling is given by

$$K = \frac{M}{\sqrt{L_p L_s}}$$

8. Draw the equivalent circuit of a pulse transformer. (Dec-13, June-14)

Ans:

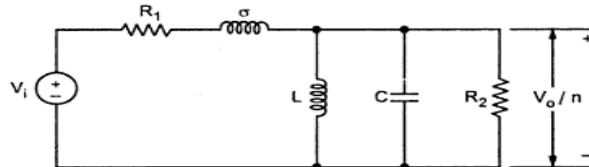**9. What is meant by linear wave shaping circuit?**

Ans: The linear network does not alter the waveform of sine wave when it is transmitted through them is known as linear wave shaping circuit.

10. Define Sweep speed error.

$$e_s = \frac{\text{Initial slope value} - \text{Final slope value}}{\text{Initial slope value}} = \frac{T_s}{RC}$$

11. Define displacement error.

Ans: It is defined as the maximum difference between the actual sweep voltage and linear sweep voltage which passes through the beginning and end points of the actual sweep.

$$e_{dis} = \frac{\delta_{max}}{V_{sweep}} = \frac{V_{S_{actual}} - V_{S_{linear}}}{V_{sweep}} = \frac{T_s}{8RC}$$

12. What is the relationship between different errors occurs in sweep generators?


Ans: $e_d = e_s/8 = e_t/4$ Where e_d is displacement error, e_t = Transmission error and e_s = Sweep speed error.

13. What is meant by a Time base generator?

Ans: Time base generator is one that provides an output which ideally rises linear with time to some predetermined value and then returns to its initial value instantaneously.


14. Draw the circuit of monostable blocking oscillator using emitter timing.

Ans:

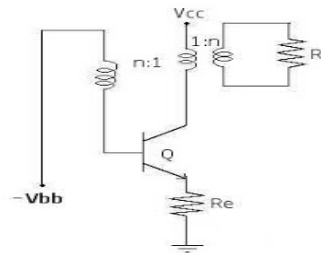

15. Draw the waveforms of UJT sawtooth generators.

Ans:

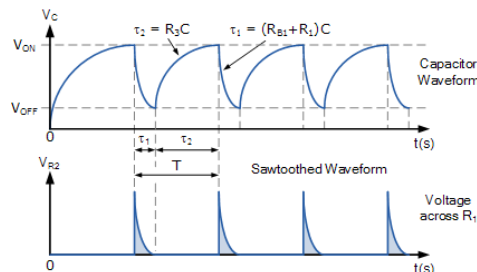

16. What are the different types of time base generators?

Ans: There are two types in Time Base generators. (1) Voltage time base generator, (2) Current Time Base Generator

17. What are the different types of Voltage time base generators?

Ans: There are three types in voltage Time Base generators namely, (i) Free running or Astable time base generator (e.g.) Bootstrap Sweep Circuit, Miller Integrator, (ii) Triggered or Monostable time base, (iii) UJT Time Base generator.

18. What is the drawback of the time base generator? How it can be eliminated?

Ans: The main drawback of the time base generator is the high percentage slope speed error. It can be reduced by improving the linearity of the sweep which is obtained by increasing supply voltage or increasing the time constant of the circuit.

19. What are the applications of time base generators? (Dec-13)

Ans: (1) It is required on the deflection plates of CRO to sweep the electron beam from left to right. (2) It is used in TV.

20. What type of feedback is used to obtain in Miller and Bootstrap circuit?


Ans: In Miller circuit the linearization is obtained by using negative feedback and in Bootstrap circuit, positive feedback is used.

21. What is 'Restoration time' and 'Sweep time' of a time base signal? (June-12)

Ans: The time, required by the voltage to reach its maximum value from its initial value, is known as sweep time and is denoted by the symbol T_s . Similarly, the time taken by the voltage to reach its initial value is called as restoration time and is denoted by the symbol T_r .

22. Draw a current sweep generator with current and voltage waveforms. (June-14)

Ans:

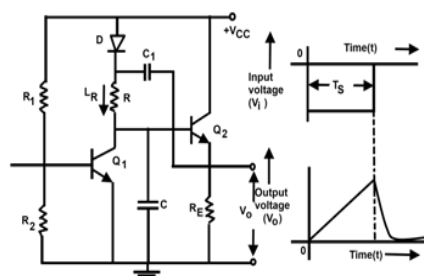

23. What is Miller theorem?

Ans: The capacitor connected in the feedback path can be divided into two capacitors, one at the input and the other at the output. This is called Miller's theorem. E.g. Miller integrator.


24. What is non-linear wave shaping?

The method of wave shaping, which make use of non-linear circuit elements such as diodes and transistors in addition to linear circuit elements are called non-linear wave shaping.

25. Mention some of the wave shaping circuits.

Ans: Differentiator, Integrator, Limiter, Clipper and Clamper.

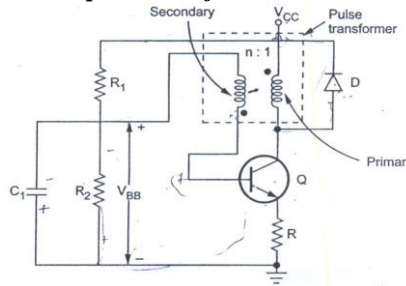26. Draw the schematic diagram for the free running oscillator.



27. What are the different methods for generation of ramp waveforms. (May 16)

a) Exponential charging b) constant current charging c) Miller Integration.

28. Mention the application of Voltage and Current Time base circuits. (Dec 15)

Ans: It is required on the deflection plates of CRO to sweep the electron beam from left to right. (2) It is used in TV and radar Systems


29. Determine the frequency of oscillation of an UJT relaxation oscillator. Assuming

$R_e=10.7K, C_e=0.22 \mu F$ and Intrinsic standoff ratio= 0.56 . (Dec 15)

Ans. $t = RC \ln[1/(1 - \eta)] = 1.932 \times 10^{-3}$

$f = 1/t = 517.59 \text{ Hz}$

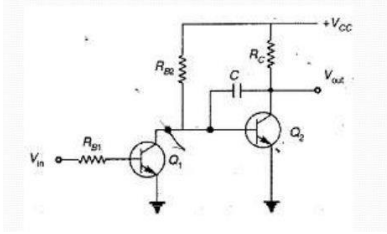30. Draw the Millers circuit to activate the sweep. (Nov 16)



31. What is known as intrinsic stand off ratio and mention its range? (Nov 16)

It is the resistive ratio of R_{B1} to the sum of R_{B1} and R_{B2} . It can be expressed as $\eta = R_{B1}/(R_{B1}+R_{B2})$ or $\eta = R_{B1}/R_{BBO}$. The typical range of intrinsic standoff ratio is from 0.4 to 0.8.

32. State any two applications of pulse transformer (May 17)

1. Change the amplitude and impedance level of a pulse. 2. Invert the polarity of the pulse. 3. Produce a pulse in a circuit having negligible d.c. resistance. 4. Differentiate a pulse. 5. Act as a coupling element in a certain pulse generating circuits.

33. Differentiate voltage and current time base circuit (May 17)

Voltage Time Base Generators – A time base generator that provides an output voltage waveform that varies linearly with time is called as a Voltage Time base Generator.

Current Time Base Generator – A time base generator that provides an output current waveform that varies linearly with time is called as a Current Time base Generator.

PART – B (C210.5)

1. Explain bootstrap time base sweep generator with circuit diagram and waveform. Derive its maximum sweep voltage, retrace interval and minimum recovery time. (June-14)
2. (i) Define slope, displacement and transmission errors with reference to a sweep signal.
(ii) With necessary waveforms and circuit diagram explain the method of generating a linear sweep voltage using Bootstrap circuit.
3. Draw the circuit for generating sweep using UJT and explain its operation. Give expression for sweep period and frequency.
4. With a neat diagram explain the operation of monostable blocking oscillator using base timing and derive pulse width (May-2015)
5. With a neat diagram explain the operation of Astable blocking oscillator with base timing. (June-12, Dec-13, Nov 16, May 17)
6. Draw and explain the operation of simple current time base generator. (Dec-13, May-2015)
7. With a neat circuit diagram and necessary waveforms, explain the concept of generating a current sweep signal.
8. With a neat circuit diagram and necessary waveforms, explain the concept of linear voltage time base generator (May-2015).
9. For a certain UJT sweep circuit, the resistance is $10K\Omega$ while the capacitance is $0.1\mu F$. The valley potential is 1.5 V when $V_{BB}=20\text{V}$. Assuming diode cut-in voltage of 0.7V and intrinsic stand-off ratio as 0.6 , calculate the frequency of oscillations. (June-12)
10. With neat circuit diagram and waveform, explain the operation of a UJT relaxation oscillator. Derive the expression for the sweep time and frequency of oscillation of the circuit. (May-2016, Nov 16, May 17)

11. Explain the operation and performance of a transistor current time base generator using a neat circuit diagram and relevant waveforms. **(May-2016)**
12. (i) With circuit diagrams and necessary waveforms, explain current sweep generator.
(ii) Define three errors that characterise the performance of time base generator. **(Dec-15)**
13. (i) Explain Astable Blocking Oscillator with Emitter timing RC controlled and derive for its frequency with circuit and waveforms.
(ii) What are advantages and disadvantages of the above blocking oscillator? **(Dec-15)**